

# REGISTER TRANSFER AND MICROOPERATIONS

- **Register Transfer Language**
- **Register Transfer**
- **Bus and Memory Transfers**
- **Arithmetic Microoperations**
- **Logic Microoperations**
- **Shift Microoperations**
- **Arithmetic Logic Shift Unit**

# SIMPLE DIGITAL SYSTEMS


- **Combinational and sequential circuits (learned in Chapters 1 and 2) can be used to create simple digital systems.**
- **These are the low-level building blocks of a digital computer.**
- **Simple digital systems are frequently characterized in terms of**
  - the registers they contain, and
  - the operations that they perform.
- **Typically,**
  - What operations are performed on the data in the registers
  - What information is passed between registers

# MICROOPERATIONS (1)

- The operations on the data in registers are called microoperations.
- The functions built into registers are examples of microoperations
  - Shift
  - Load
  - Clear
  - Increment
  - ...
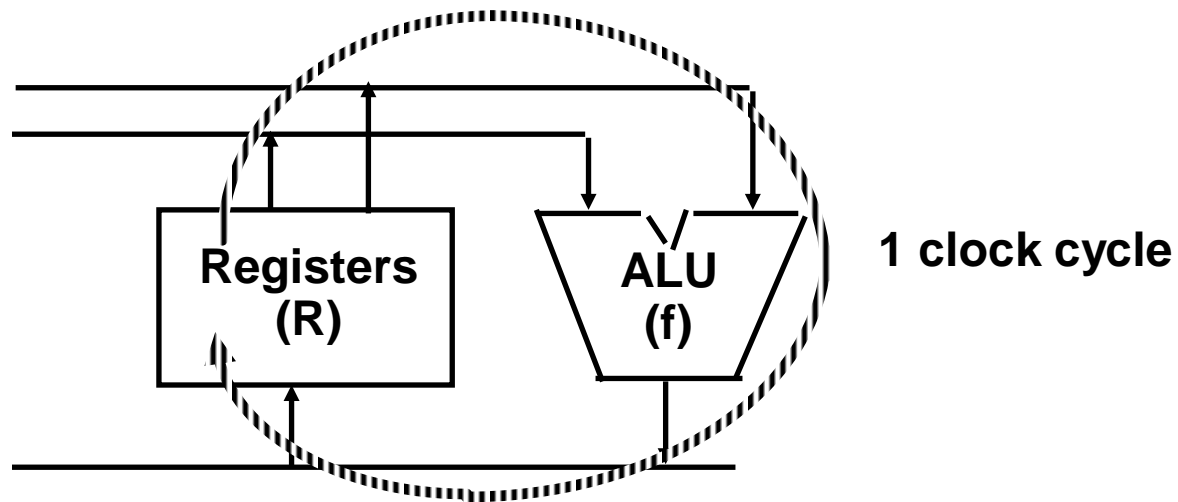
## MICROOPERATION (2)

An elementary operation performed (during one clock pulse), on the information stored in one or more registers



$$R \leftarrow f(R, R)$$

**f:** shift, load, clear, increment, add, subtract, complement, and, or, xor, ...

# ORGANIZATION OF A DIGITAL SYSTEM

- **Definition of the (internal) organization of a computer**
  - **Set of registers and their functions**
  - **Microoperations set**  
  
**Set of allowable microoperations provided by the organization of the computer**
  - **Control signals that initiate the sequence of microoperations (to perform the functions)**

# REGISTER TRANSFER LEVEL

- Viewing a computer, or any digital system, in this way is called the register transfer level
- This is because we're focusing on
  - The system's registers
  - The data transformations in them, and
  - The data transfers between them.

# REGISTER TRANSFER LANGUAGE

- Rather than specifying a digital system in words, a specific notation is used, *register transfer language*
- For any function of the computer, the register transfer language can be used to describe the (sequence of) microoperations
- Register transfer language
  - A symbolic language
  - A convenient tool for describing the internal organization of digital computers
  - Can also be used to facilitate the design process of digital systems.

# DESIGNATION OF REGISTERS

- Registers are designated by capital letters, sometimes followed by numbers (e.g., A, R13, IR)
- Often the names indicate function:
  - MAR      - memory address register
  - PC        - program counter
  - IR        - instruction register
- Registers and their contents can be viewed and represented in *various ways*
  - A register can be viewed as a single entity:



- Registers may also be represented showing the bits of data they contain



# DESIGNATION OF REGISTERS

- Designation of a register
  - a register
  - portion of a register
  - a bit of a register
  
- Common ways of drawing the block diagram of a register

Register




15

0



Numbering of bits

Showing individual bits

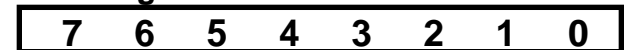

15

8 7

0



Subfields

# REGISTER TRANSFER

- Copying the contents of one register to another is a register transfer
- A register transfer is indicated as

**$R2 \leftarrow R1$**

- In this case the contents of register R2 are copied (loaded) from register R1
- A simultaneous transfer of all bits from the source R1 to the destination register R2, during one clock pulse
- Note that this is non-destructive; i.e. the contents of R1 are not altered by copying (loading) them to R2

# REGISTER TRANSFER

- A register transfer such as

**$R3 \leftarrow R5$**

**Implies that the digital system has**

- the data lines from the source register (R5) to the destination register (R3)
- Parallel load in the destination register (R3)
- Control lines to perform the action

# CONTROL FUNCTIONS

- Often actions need to only occur if a certain condition is true
- This is similar to an “if” statement in a programming language
- In digital systems, this is often done via a *control signal*, called a *control function*
  - If the signal is 1, the action takes place
- This is represented as:

**P:  $R2 \leftarrow R1$**


Which means “if  $P = 1$ , then load the contents of register R1 into register R2”, i.e., if  $(P = 1)$  then  $(R2 \leftarrow R1)$

# HARDWARE IMPLEMENTATION OF CONTROLLED TRANSFERS


## Implementation of controlled transfer

P:  $R2 \leftarrow R1$

### Block diagram

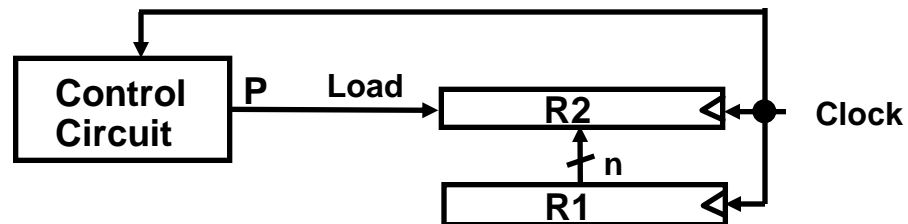

### Timing diagram

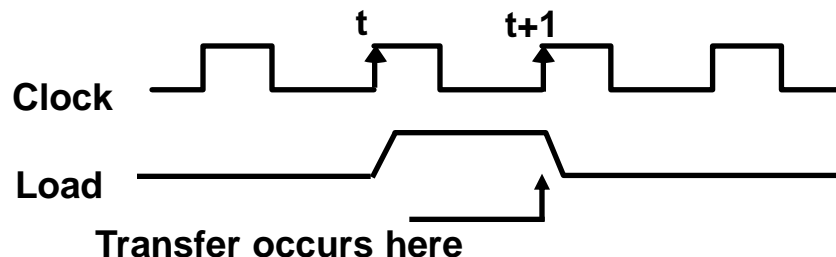

- The same clock controls the circuits that generate the control function and the destination register
- Registers are assumed to use *positive-edge-triggered* flip-flops

# SIMULTANEOUS OPERATIONS

- If two or more operations are to occur simultaneously, they are separated with commas

**P:  $R3 \leftarrow R5, MAR \leftarrow IR$**

- Here, if the control function  $P = 1$ , load the contents of R5 into R3, and at the same time (clock), load the contents of register IR into register MAR

# BASIC SYMBOLS FOR REGISTER TRANSFERS

Symbols	Description	Examples
Capital letters & numerals	Denotes a register	MAR, R2
Parentheses ()	Denotes a part of a register	R2(0-7), R2(L)
Arrow $\leftarrow$	Denotes transfer of information	R2 $\leftarrow$ R1
Colon :	Denotes termination of control function	P:
Comma ,	Separates two micro-operations	A $\leftarrow$ B, B $\leftarrow$ A

# CONNECTING REGISTERS



- In a digital system with many registers, it is impractical to have data and control lines to directly allow each register to be loaded with the contents of every possible other registers
- To completely connect  $n$  registers  $\rightarrow n(n-1)$  lines
- $O(n^2)$  cost
  - This is not a realistic approach to use in a large digital system
- Instead, take a different approach
- Have one centralized set of circuits for data transfer – the **bus**
- Have control circuits to select which register is the source, and which is the destination



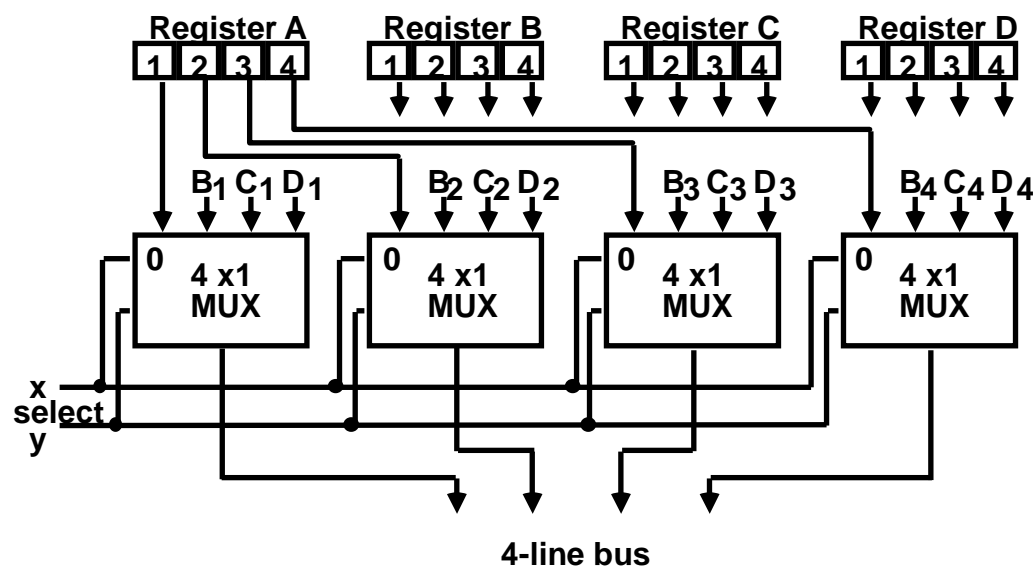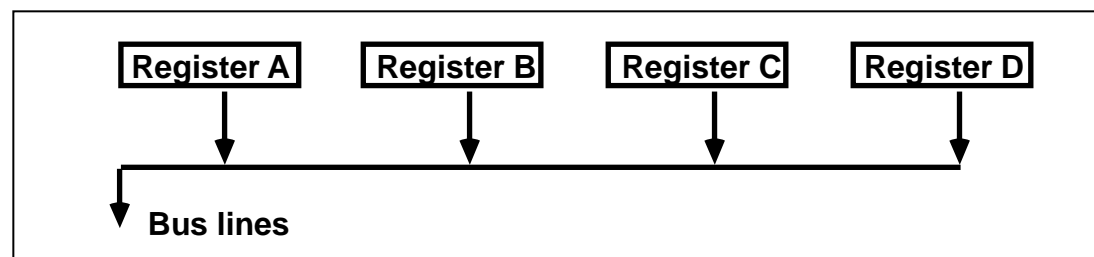
# BUS AND BUS TRANSFER

Bus is a path(of a group of wires) over which information is transferred, from any of several sources to any of several destinations.

From a register to bus:  $BUS \leftarrow R$


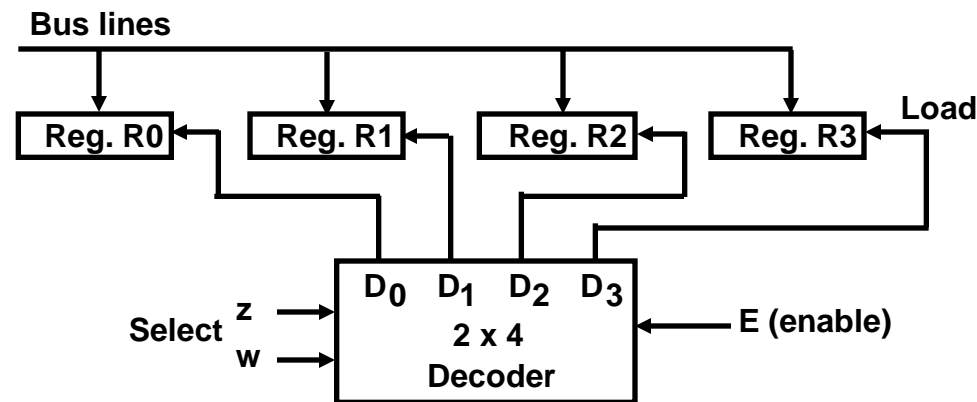
# TRANSFER FROM BUS TO A DESTINATION REGISTER




## Three-State Bus Buffers

Normal input A  
Control input C



Output Y=A if C=1  
High-impedence if C=0

## Bus line with three-state buffers

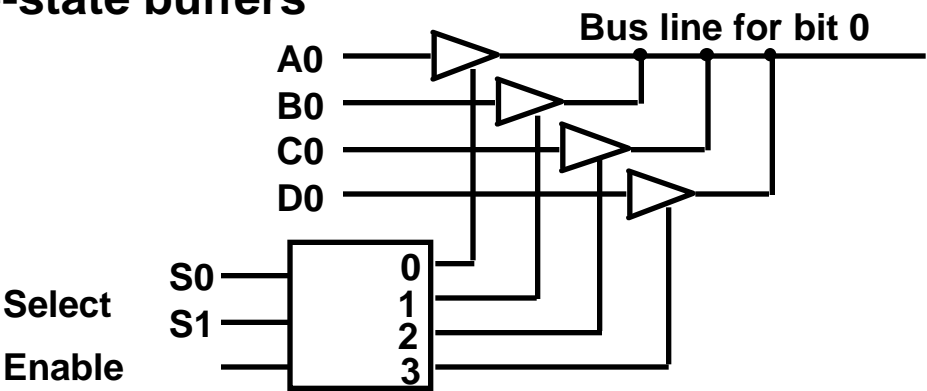

# BUS TRANSFER IN RTL

- Depending on whether the bus is to be mentioned explicitly or not, register transfer can be indicated as either

$R2 \leftarrow R1$


or

$BUS \leftarrow R1, R2 \leftarrow BUS$

- In the former case the bus is implicit, but in the latter, it is explicitly indicated

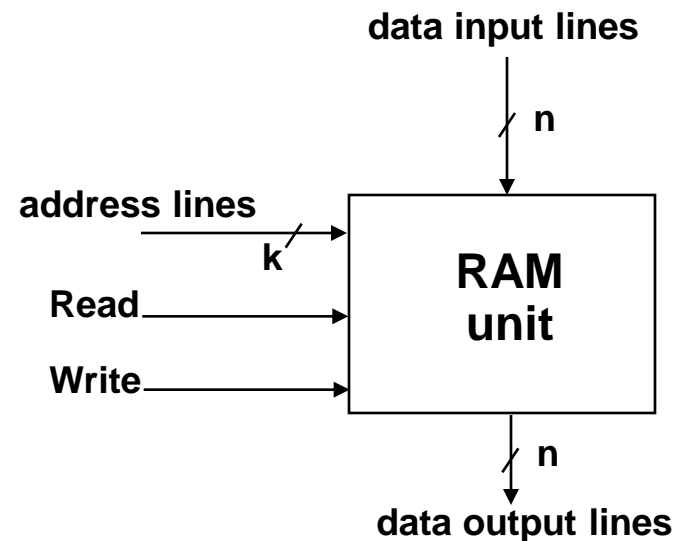
# MEMORY (RAM)

- Memory (RAM) can be thought as a sequential circuits containing some number of registers
- These registers hold the *words* of memory
- Each of the  $r$  registers is indicated by an *address*
- These addresses range from 0 to  $r-1$
- Each register (word) can hold  $n$  bits of data
- Assume the RAM contains  $r = 2^k$  words. It needs the following
  - $n$  data input lines
  - $n$  data output lines
  - $k$  address lines
  - A Read control line
  - A Write control line


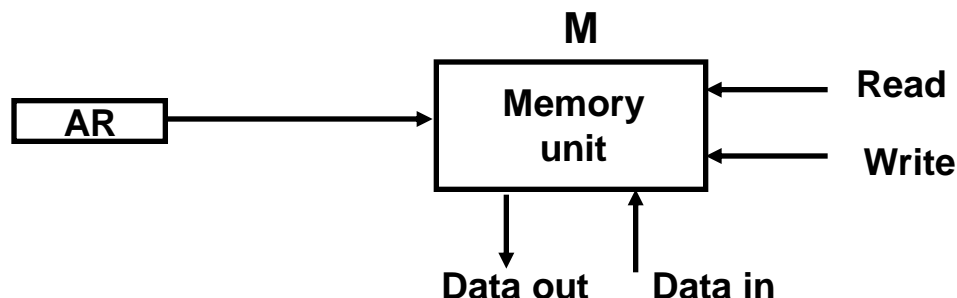
# MEMORY TRANSFER

- Collectively, the memory is viewed at the register level as a device, M.
- Since it contains multiple locations, we must specify which address in memory we will be using
- This is done by indexing memory references
- Memory is usually accessed in computer systems by putting the desired address in a special register, the *Memory Address Register (MAR, or AR)*
- When memory is accessed, the contents of the MAR get sent to the memory unit's address lines



# MEMORY READ

- To read a value from a location in memory and load it into a register, the register transfer language notation looks like this:

**$R1 \leftarrow M[MAR]$**

- This causes the following to occur
  - The contents of the MAR get sent to the memory address lines
  - A Read (= 1) gets sent to the memory unit
  - The contents of the specified address are put on the memory's output data lines
  - These get sent over the bus to be loaded into register R1

# MEMORY WRITE

- To write a value from a register to a location in memory looks like this in register transfer language:

**$M[MAR] \leftarrow R1$**

- This causes the following to occur
  - The contents of the MAR get sent to the memory address lines
  - A Write (= 1) gets sent to the memory unit
  - The values in register R1 get sent over the bus to the data input lines of the memory
  - The values get loaded into the specified address in the memory

# SUMMARY OF R. TRANSFER MICROOPERATIONS

**$A \leftarrow B$**

**Transfer content of reg. B into reg. A**

**$AR \leftarrow DR(AD)$**

**Transfer content of AD portion of reg. DR into reg. AR**

**$A \leftarrow \text{constant}$**

**Transfer a binary constant into reg. A**

**$ABUS \leftarrow R1,$**

**Transfer content of R1 into bus A and, at the same time,  
transfer content of bus A into R2**

**$R2 \leftarrow ABUS$**

**AR**

**Address register**

**DR**

**Data register**

**$M[R]$**

**Memory word specified by reg. R**

**M**

**Equivalent to  $M[AR]$**

**$DR \leftarrow M$**

**Memory *read* operation: transfers content of  
memory word specified by AR into DR**

**$M \leftarrow DR$**

**Memory *write* operation: transfers content of  
DR into memory word specified by AR**



# **MICROOPERATIONS**

- **Computer system microoperations are of four types:**
  - **Register transfer microoperations**
  - **Arithmetic microoperations**
  - **Logic microoperations**
  - **Shift microoperations**

# ARITHMETIC MICROOPERATIONS


- The basic arithmetic microoperations are
  - Addition
  - Subtraction
  - Increment
  - Decrement
- The additional arithmetic microoperations are
  - Add with carry
  - Subtract with borrow
  - Transfer/Load
  - etc. ...

## Summary of Typical Arithmetic Micro-Operations


$R3 \leftarrow R1 + R2$	Contents of R1 plus R2 transferred to R3
$R3 \leftarrow R1 - R2$	Contents of R1 minus R2 transferred to R3
$R2 \leftarrow R2'$	Complement the contents of R2
$R2 \leftarrow R2' + 1$	2's complement the contents of R2 (negate)
$R3 \leftarrow R1 + R2' + 1$	subtraction
$R1 \leftarrow R1 + 1$	Increment
$R1 \leftarrow R1 - 1$	Decrement

# BINARY ADDER / SUBTRACTOR / INCREMENTER


## Binary Adder

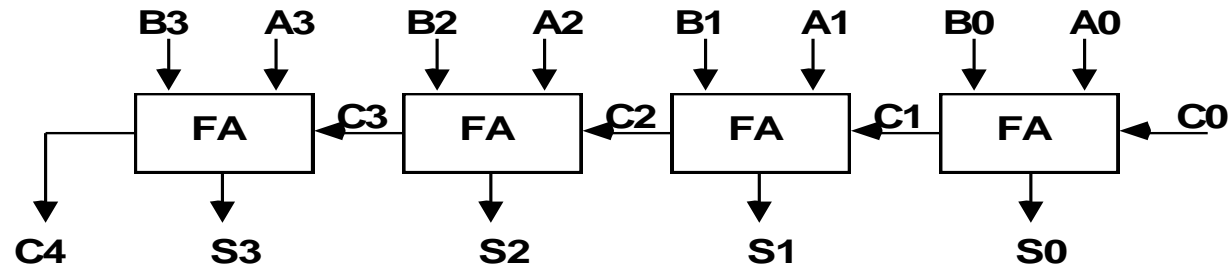


## Binary Adder-Subtractor

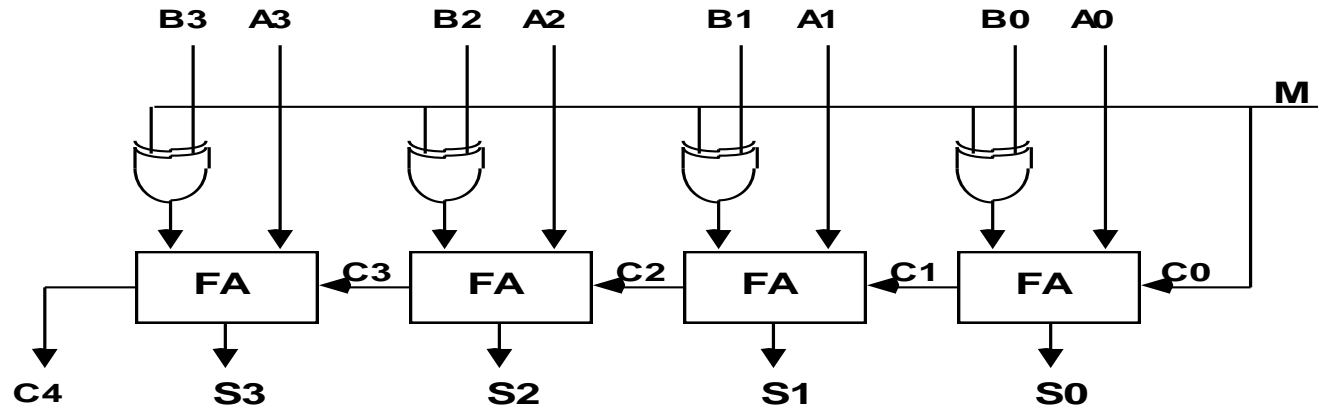

## Binary Incrementer

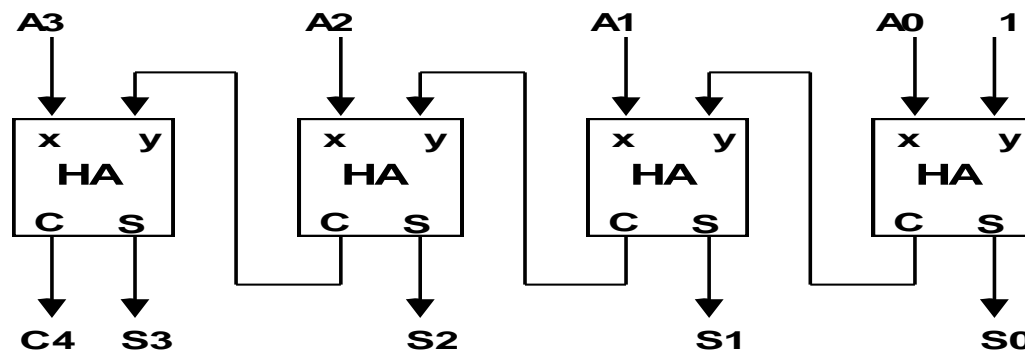

# ARITHMETIC CIRCUIT

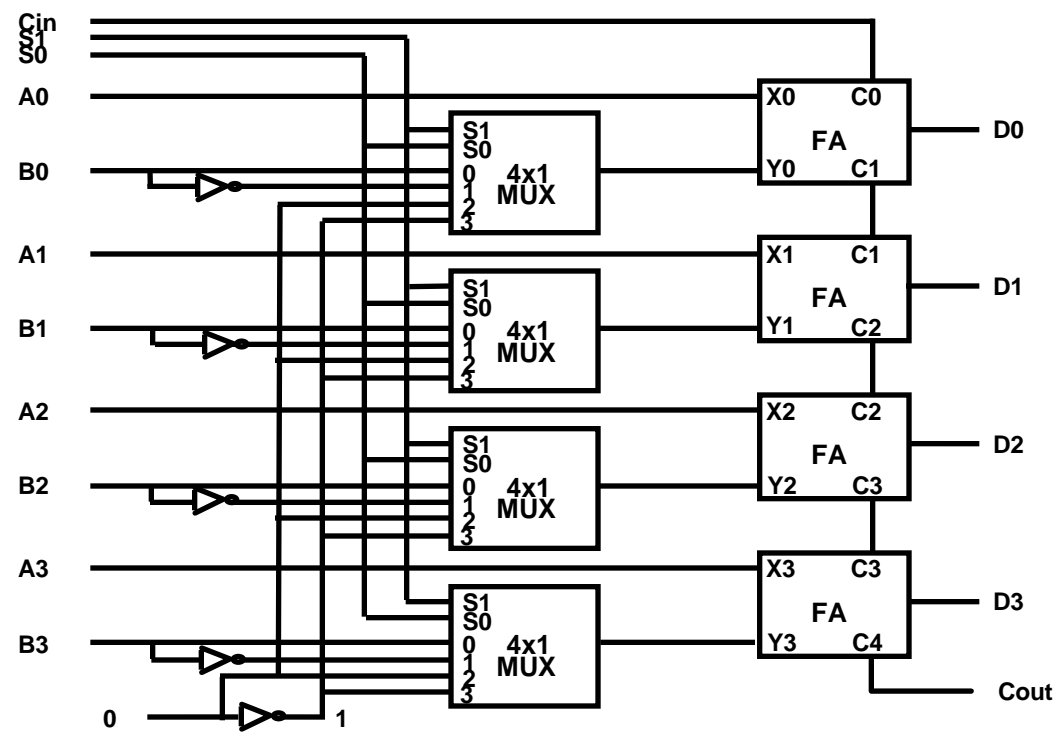

S1	S0	Cin	Y	Output	Microoperation
0	0	0	B	$D = A + B$	Add
0	0	1	B	$D = A + B + 1$	Add with carry
0	1	0	$B'$	$D = A + B'$	Subtract with borrow
0	1	1	$B'$	$D = A + B' + 1$	Subtract
1	0	0	0	$D = A$	Transfer A
1	0	1	0	$D = A + 1$	Increment A
1	1	0	1	$D = A - 1$	Decrement A
1	1	1	1	$D = A$	Transfer A

# LOGIC MICROOPERATIONS

- **Specify binary operations on the strings of bits in registers**
  - Logic microoperations are bit-wise operations, i.e., they work on the individual bits of data
  - useful for bit manipulations on binary data
  - useful for making logical decisions based on the bit value
- **There are, in principle, 16 different logic functions that can be defined over two binary input variables**

A	B	$F_0$	$F_1$	$F_2 \dots F_{13}$	$F_{14}$	$F_{15}$
0	0	0	0	0 ... 1	1	1
0	1	0	0	0 ... 1	1	1
1	0	0	0	1 ... 0	1	1
1	1	0	1	0 ... 1	0	1


- **However, most systems only implement four of these**
  - AND ( $\wedge$ ), OR ( $\vee$ ), XOR ( $\oplus$ ), Complement/NOT
- **The others can be created from combination of these**

# LIST OF LOGIC MICROOPERATIONS

- List of Logic Microoperations
  - 16 different logic operations with 2 binary vars.
  - n binary vars  $\rightarrow 2^{2^n}$  functions
- Truth tables for 16 functions of 2 variables and the corresponding 16 logic micro-operations

x	0 0 1 1	<i>Boolean Function</i>	<i>Micro-Operations</i>	<i>Name</i>
y	0 1 0 1			
	0 0 0 0	$F_0 = 0$	$F \leftarrow 0$	Clear
	0 0 0 1	$F_1 = xy$	$F \leftarrow A \wedge B$	AND
	0 0 1 0	$F_2 = xy'$	$F \leftarrow A \wedge B'$	
	0 0 1 1	$F_3 = x$	$F \leftarrow A$	Transfer A
	0 1 0 0	$F_4 = x'y$	$F \leftarrow A' \wedge B$	
	0 1 0 1	$F_5 = y$	$F \leftarrow B$	Transfer B
	0 1 1 0	$F_6 = x \oplus y$	$F \leftarrow A \oplus B$	Exclusive-OR
	0 1 1 1	$F_7 = x + y$	$F \leftarrow A \vee B$	OR
	1 0 0 0	$F_8 = (x + y)'$	$F \leftarrow (A \vee B)'$	NOR
	1 0 0 1	$F_9 = (x \oplus y)'$	$F \leftarrow (A \oplus B)'$	Exclusive-NOR
	1 0 1 0	$F_{10} = y'$	$F \leftarrow B'$	Complement B
	1 0 1 1	$F_{11} = x + y'$	$F \leftarrow A \vee B$	
	1 1 0 0	$F_{12} = x'$	$F \leftarrow A'$	Complement A
	1 1 0 1	$F_{13} = x' + y$	$F \leftarrow A' \vee B$	
	1 1 1 0	$F_{14} = (xy)'$	$F \leftarrow (A \wedge B)'$	NAND
	1 1 1 1	$F_{15} = 1$	$F \leftarrow \text{all 1's}$	Set to all 1's

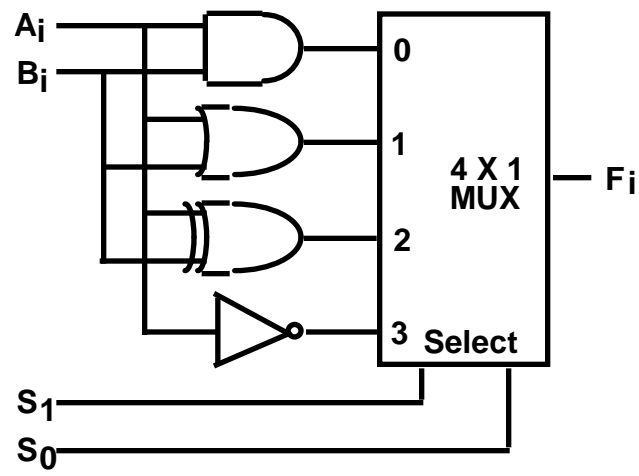**HARDWARE IMPLEMENTATION OF LOGIC MICROOPERATIONS**



**Function table**

$S_1$	$S_0$	Output	$\mu$ -operation
0	0	$F = A \wedge B$	AND
0	1	$F = A \vee B$	OR
1	0	$F = A \oplus B$	XOR
1	1	$F = A'$	Complement

# APPLICATIONS OF LOGIC MICROOPERATIONS

- Logic microoperations can be used to manipulate individual bits or a portions of a word in a register
- Consider the data in a register A. In another register, B, is bit data that will be used to modify the contents of A

- |                        |                                |
|------------------------|--------------------------------|
| – Selective-set        | $A \leftarrow A + B$           |
| – Selective-complement | $A \leftarrow A \oplus B$      |
| – Selective-clear      | $A \leftarrow A \cdot B'$      |
| – Mask (Delete)        | $A \leftarrow A \cdot B$       |
| – Clear                | $A \leftarrow A \oplus B$      |
| – Insert               | $A \leftarrow (A \cdot B) + C$ |
| – Compare              | $A \leftarrow A \oplus B$      |
| – ...                  |                                |



# SELECTIVE SET

- In a selective set operation, the bit pattern in B is used to set certain bits in A

1 1 0 0	$A_t$	
1 0 1 0	B	
<hr/>		
1 1 1 0	$A_{t+1}$	$(A \leftarrow A + B)$

- If a bit in B is set to 1, that same position in A gets set to 1, otherwise that bit in A keeps its previous value

# SELECTIVE COMPLEMENT

- In a selective complement operation, the bit pattern in B is used to *complement* certain bits in A

1 1 0 0	$A_t$	
1 0 1 0	B	
<hr/>		
0 1 1 0	$A_{t+1}$	$(A \leftarrow A \oplus B)$

- If a bit in B is set to 1, that same position in A gets complemented from its original value, otherwise it is unchanged

# SELECTIVE CLEAR

- In a selective clear operation, the bit pattern in B is used to *clear* certain bits in A

1 1 0 0	$A_t$	
1 0 1 0	B	
<hr/>		
0 1 0 0	$A_{t+1}$	$(A \leftarrow A \cdot B')$

- If a bit in B is set to 1, that same position in A gets set to 0, otherwise it is unchanged

# MASK OPERATION

- In a mask operation, the bit pattern in B is used to *clear* certain bits in A

1 1 0 0	$A_t$	
1 0 1 0	B	
<hr/>		
1 0 0 0	$A_{t+1}$	$(A \leftarrow A \cdot B)$

- If a bit in B is set to 0, that same position in A gets set to 0, otherwise it is unchanged

# CLEAR OPERATION

- In a clear operation, if the bits in the same position in A and B are the same, they are cleared in A, otherwise they are set in A

1 1 0 0	$A_t$	
1 0 1 0	B	
<hr/>		
0 1 1 0	$A_{t+1}$	$(A \leftarrow A \oplus B)$

# INSERT OPERATION


- An insert operation is used to introduce a specific bit pattern into A register, leaving the other bit positions unchanged
- This is done as
  - A mask operation to clear the desired bit positions, followed by
  - An OR operation to introduce the new bits into the desired positions
  - Example
    - » Suppose you wanted to introduce 1010 into the low order four bits of A:
 

1101 1000 1011 0001	A (Original)
1101 1000 1011 1010	A (Desired)


» 1101 1000 1011 0001	A (Original)
1111 1111 1111 0000	Mask
<hr/>	
1101 1000 1011 0000	A (Intermediate)
0000 0000 0000 1010	Added bits
<hr/>	
1101 1000 1011 1010	A (Desired)
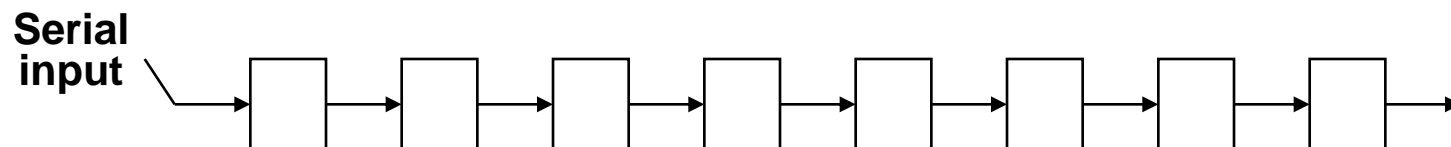
# SHIFT MICROOPERATIONS

- There are three types of shifts
  - *Logical shift*
  - *Circular shift*
  - *Arithmetic shift*
- What differentiates them is the information that goes into the serial input
- A right shift operation




- A left shift operation

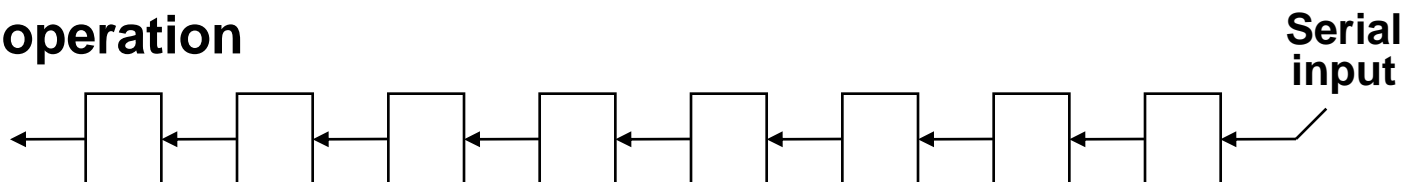

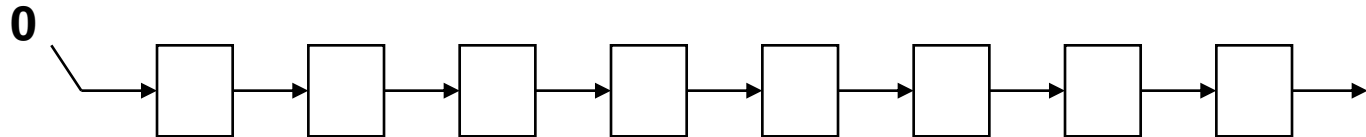
# LOGICAL SHIFT

- In a logical shift the serial input to the shift is a 0.
- A right logical shift operation:



- A left logical shift operation:

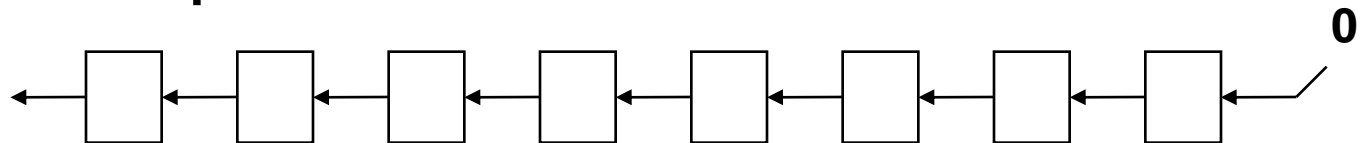


- In a Register Transfer Language, the following notation is used
  - *shl* for a logical shift left
  - *shr* for a logical shift right
  - Examples:
    - »  $R2 \leftarrow shr\ R2$
    - »  $R3 \leftarrow shl\ R3$




# CIRCULAR SHIFT

- In a circular shift the serial input is the bit that is shifted out of the other end of the register.

- A right circular shift operation:

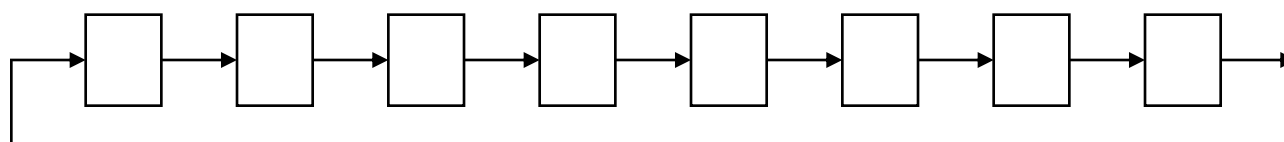


- A left circular shift operation:

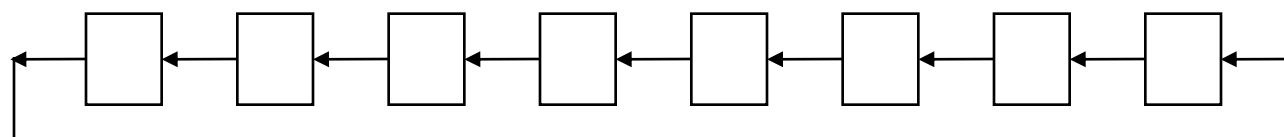


- In a RTL, the following notation is used
  - *cil* for a circular shift left
  - *cir* for a circular shift right
  - Examples:
    - »  $R2 \leftarrow cir\ R2$
    - »  $R3 \leftarrow cil\ R3$
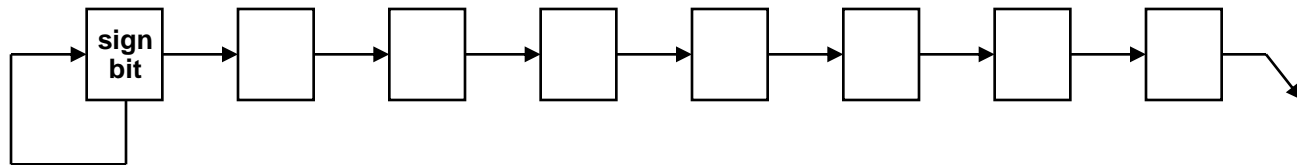
# ARITHMETIC SHIFT

- An arithmetic shift is meant for signed binary numbers (integer)
- An arithmetic left shift **multiplies** a signed number **by two**
- An arithmetic right shift **divides** a signed number **by two**
- The main distinction of an arithmetic shift is that it must keep the sign of the number the same as it performs the multiplication or division
- A right arithmetic shift operation:




- A left arithmetic shift operation:

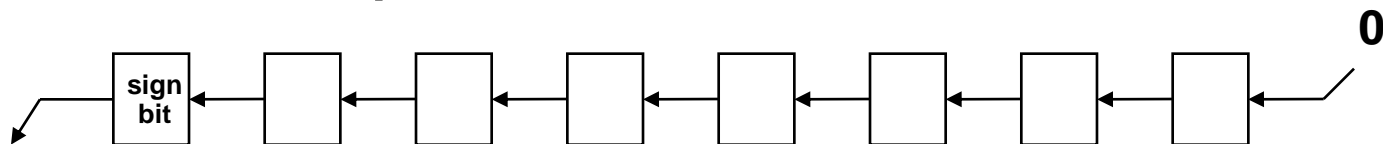

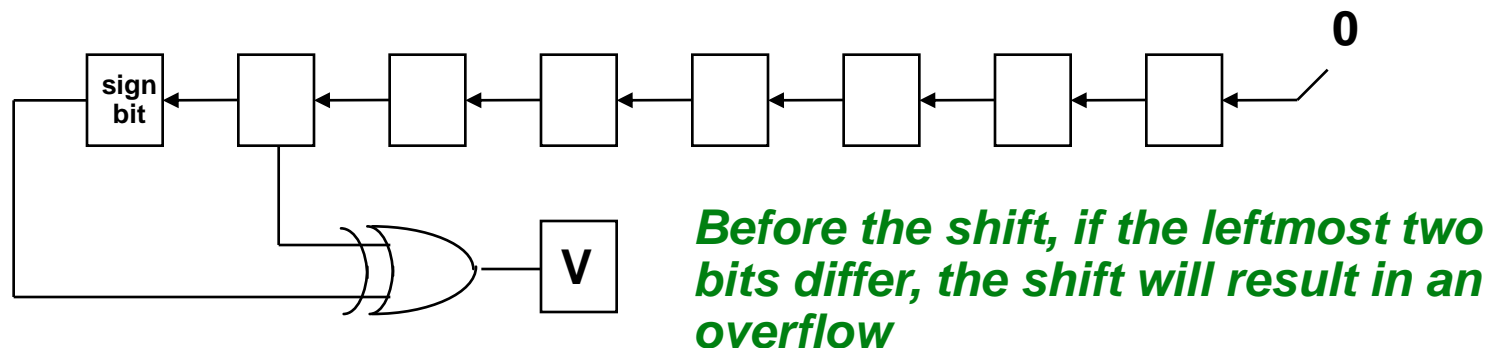
# ARITHMETIC SHIFT

- An left arithmetic shift operation must be checked for the **overflow**




- In a RTL, the following notation is used
  - *ashl* for an arithmetic shift left
  - *ashr* for an arithmetic shift right
  - Examples:
    - »  $R2 \leftarrow ashr R2$
    - »  $R3 \leftarrow ashl R3$

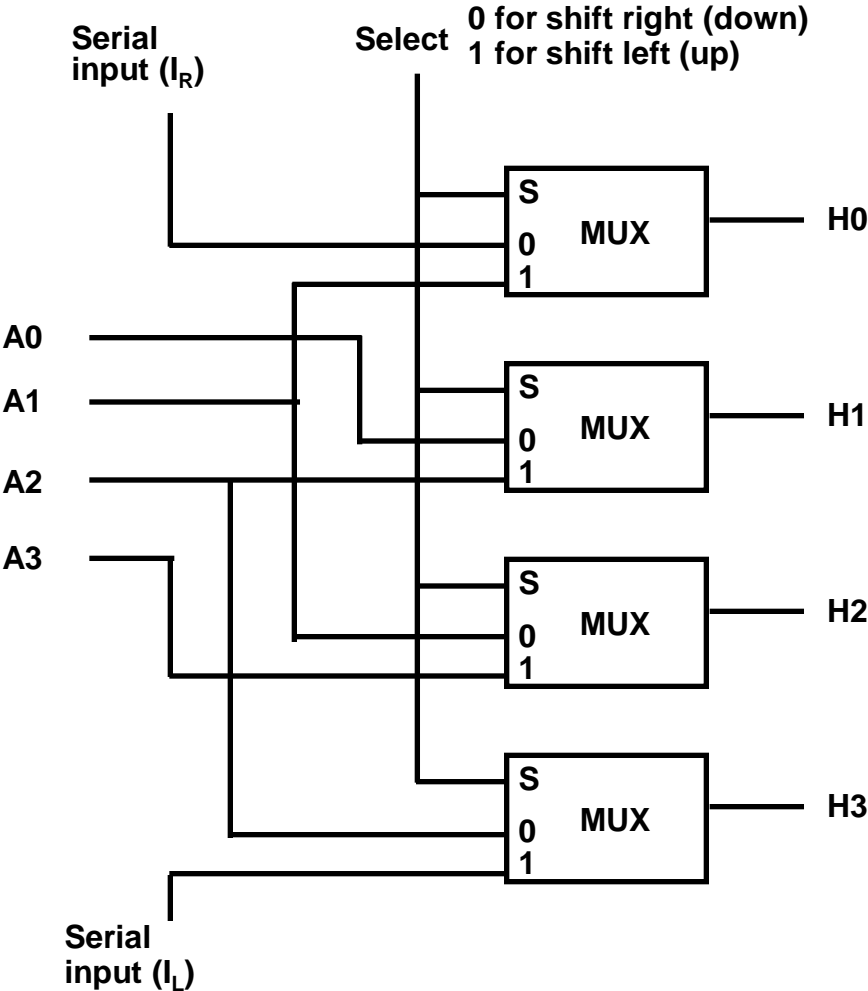**HARDWARE IMPLEMENTATION OF SHIFT MICROOPERATIONS**



# ARITHMETIC LOGIC SHIFT UNIT

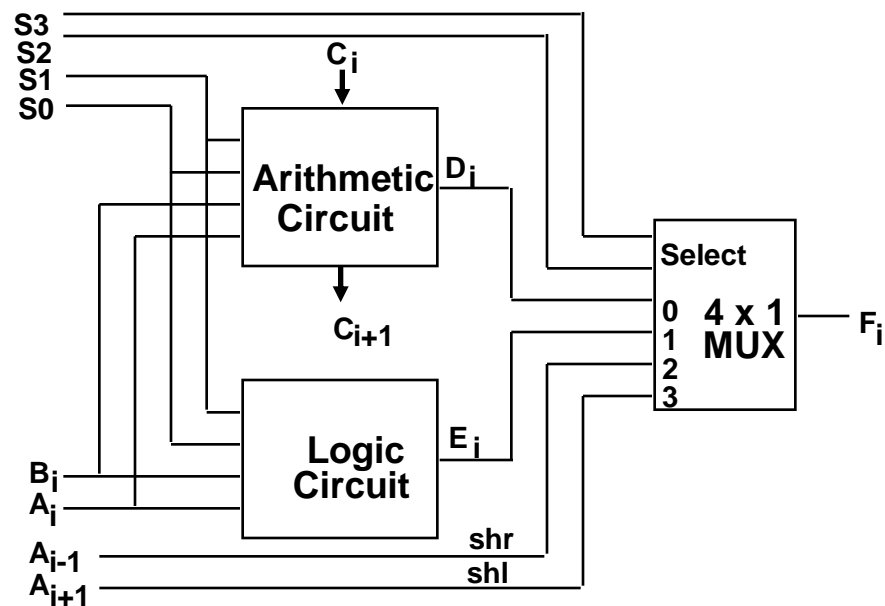

S3	S2	S1	S0	Cin	Operation	Function
0	0	0	0	0	$F = A$	Transfer A
0	0	0	0	1	$F = A + 1$	Increment A
0	0	0	1	0	$F = A + B$	Addition
0	0	0	1	1	$F = A + B + 1$	Add with carry
0	0	1	0	0	$F = A + B'$	Subtract with borrow
0	0	1	0	1	$F = A + B' + 1$	Subtraction
0	0	1	1	0	$F = A - 1$	Decrement A
0	0	1	1	1	$F = A$	Transfer A
0	1	0	0	X	$F = A \wedge B$	AND
0	1	0	1	X	$F = A \vee B$	OR
0	1	1	0	X	$F = A \oplus B$	XOR
0	1	1	1	X	$F = A'$	Complement A
1	0	X	X	X	$F = \text{shr } A$	Shift right A into F
1	1	X	X	X	$F = \text{shl } A$	Shift left A into F